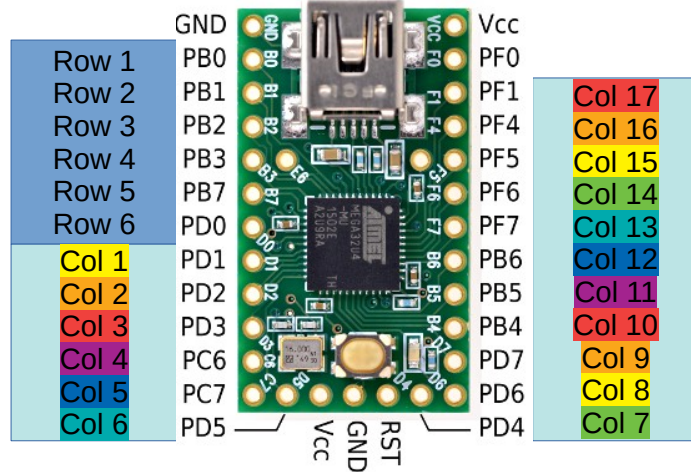


andimoto smallTKL iso wiring diagram

https://www.pjrc.com/teensy/card2a_rev5_web.pdf



Note: This wiring is very wastful. As the Teensy 2.0 has enough pins available, I could do a direct wiring. This keyboard could also use a Arduino Pro Micro. The wiring of the smallTKL ANSI layout could be adopted for this ISO layout easily.

Wiring: Solder each line of „Rows“ and each line of „Columns“ to controller as described in diagram.

Set soldering iron to about 315°C. Also see wiring help from QMK documentation. For connections directly to controller use thin wires. Otherwise the will be not much space to close the case.

Note: Case diagram is upside-down!

